

ECE159 Notes

QiLin Xue

January 14, 2021

Contents

1 Foundation 1

1 Foundation

- Electric current describes the rate of *positive* charge flow¹:

$$i(t) = \frac{dq}{dt} \quad (1)$$

and is measured in amperes [A]. The charge Q that passes a given point is:


$$Q = \int_{t_0}^t i \, dt \quad (2)$$

and is measured in coulombs [C].


- Voltage describes the electric potential difference across the element:

$$V_{ab} = \frac{dW}{dq} \quad (3)$$

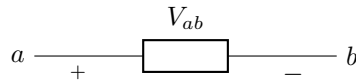which is physically described as the work required to move a unit positive charge of +1C from b to a . It is measured in volts [V].



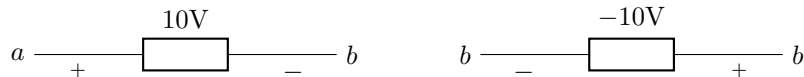Notice that the below two setups are equivalent:



- Power is the rate of energy flow:

$$P = V \cdot I \quad (4)$$


Energy produced by the battery and the current generated runs through the bulb and the energy is dissipated into heat and light. Measured in watts [W]. We show this is true from the classical definition of power:

$$P = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} = V \cdot i \quad (5)$$

- In a DC (direct current) circuit, current flows in one direction and is constant with respect to time. In an AC (alternating current) circuit, the current varies direction with respect to time.
- To distinguish between supplying or absorbing power, we use passive sign convention:

¹<https://xkcd.com/567/>

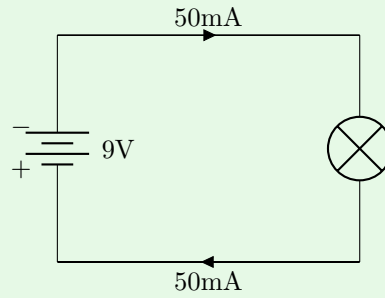Definition: If power is positive, the element absorbs power and if negative, the element supplies power. Take the following circuit for example:



and we will get:

$$P_{\text{bulb}} = +iV = +0.45\text{W}, \text{ (absorbing)} \quad (6)$$

$$P_{\text{battery}} = -iV = -0.45\text{W}, \text{ (supplying)} \quad (7)$$

which gives:

$$\sum P = 0 \quad (8)$$